

FORZA ELETTROMOTRICE

$$\Delta V = Ri = V_A - V_B = \int_A^B \vec{E} \cdot d\vec{s}$$

$$\oint \vec{E} \cdot d\vec{s} = Ri \neq 0, \quad \vec{E} = \vec{E}_{el} + \vec{E}_{em}$$

$$\oint \cancel{\vec{E}_{el} \cdot d\vec{s}} + \underbrace{\oint \vec{E}_{em} \cdot d\vec{s}}_{\varepsilon} = Ri$$

ε FORZA ELETTROMOTRICE


CAMPO
ELETTROMOTORE

$$[\varepsilon] = V \text{ Volt}$$



$$\Delta V = Ri \text{ legge di Ohm}$$

↓
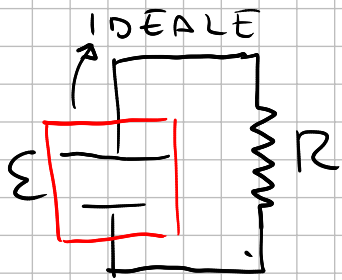
$$\varepsilon = Ri \text{ in presenza di generatori}$$




INTERPRETAZIONE FISICA
GENERATORE REALE

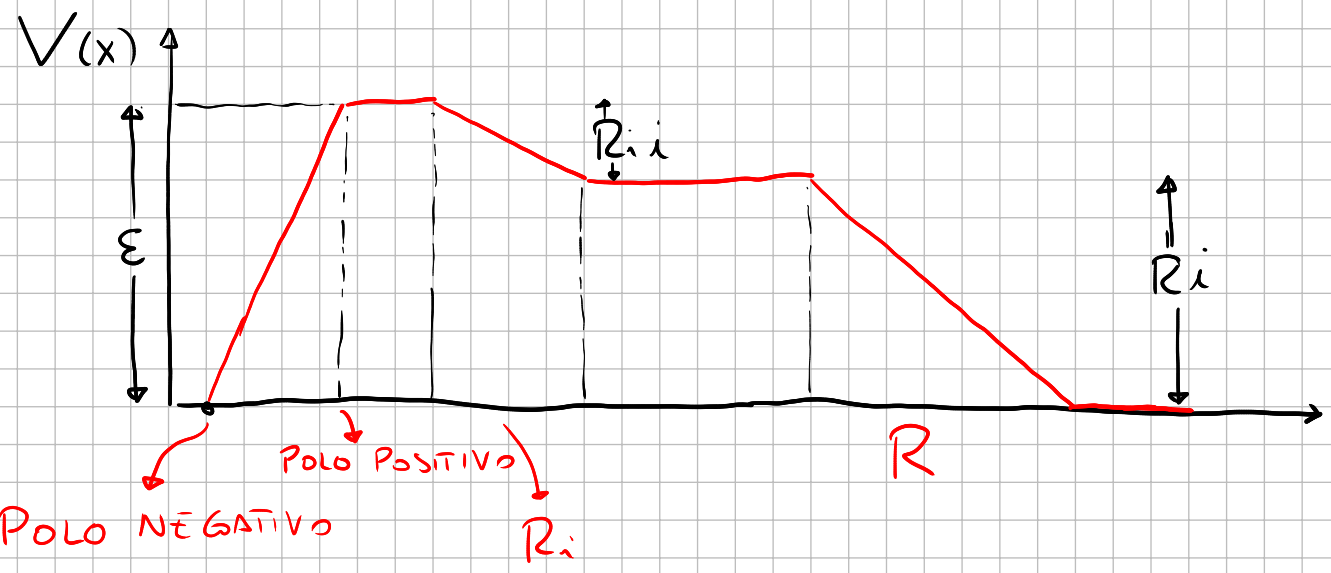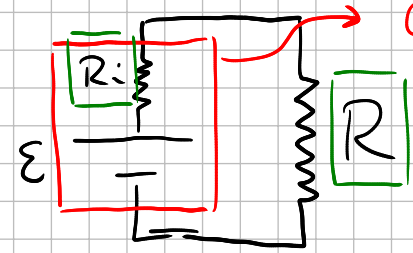

$$U_e = q_0 V$$

CIRCUITO RC

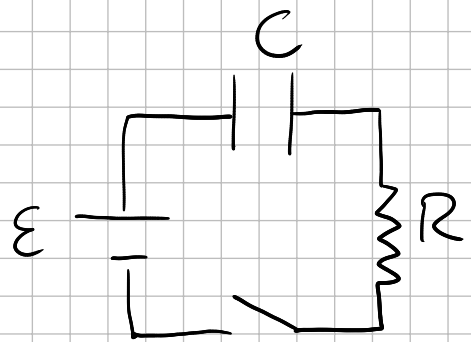

$$\Delta V_C = \frac{q}{C}, \quad \Delta V_R = Ri, \quad \varepsilon$$

$$\varepsilon = \Delta V_C + \Delta V_R = \frac{q}{C} + Ri = \frac{q}{C} + R \frac{dq}{dt} \Rightarrow$$


$$R \frac{dq}{dt} = \varepsilon - \frac{q}{C} \Rightarrow \frac{dq}{C\varepsilon - q} = \frac{dt}{RC} \Rightarrow \frac{dq}{q - C\varepsilon} = -\frac{dt}{RC} \Rightarrow$$

$$\int_0^{q(t)} \frac{dq'}{q' - C\varepsilon} = \int_0^t -\frac{dt}{RC} = -\frac{t}{RC} \Rightarrow \int_0^{q(t)} \frac{dq'}{q' - C\varepsilon} = \log(q' - C\varepsilon) \Big|_0^{q(t)} = \log(q(t) - C\varepsilon) - \log(-C\varepsilon)$$

$$\Rightarrow \log \left[\frac{q(t) - C\varepsilon}{-C\varepsilon} \right] = -\frac{t}{RC} \Rightarrow \frac{q(t) - C\varepsilon}{-C\varepsilon} = e^{-\frac{t}{RC}} \Rightarrow$$

$$q(t) = C\varepsilon \left(1 - e^{-\frac{t}{RC}} \right)$$
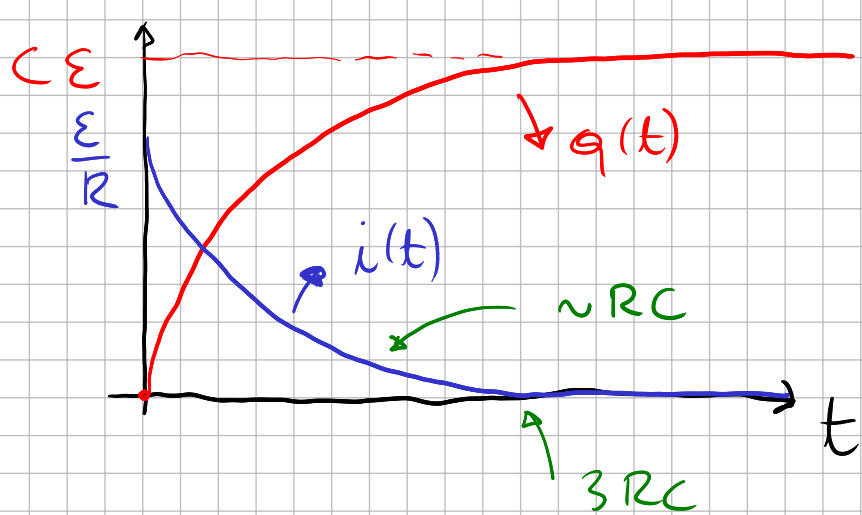
$$q(t) = C\varepsilon(1 - e^{-\frac{t}{RC}}), \quad i(t) = \frac{\varepsilon}{R} e^{-\frac{t}{RC}}, \quad \Delta V_c = \varepsilon(1 - e^{-\frac{t}{RC}})$$



$$e^{-\frac{t}{RC}}$$


$$[RC] = \text{D}$$

RC TEMPO CARATTERISTICO

$$RC = \tau$$


$$W = \int_0^{C\varepsilon} \varepsilon dq = \varepsilon^2 C, \quad U_e^{(c)} = \frac{1}{2} \varepsilon^2 C, \quad W - U_e^{(c)} = \frac{1}{2} \varepsilon^2 C$$

SCARICA DI UN CONDENSATORE

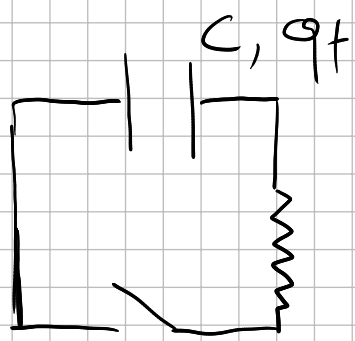

$$\Delta V_R + \Delta V_C = 0 \Rightarrow Ri + \frac{q}{C} = R \frac{dq}{dt} + \frac{q}{C} = 0 \Rightarrow$$
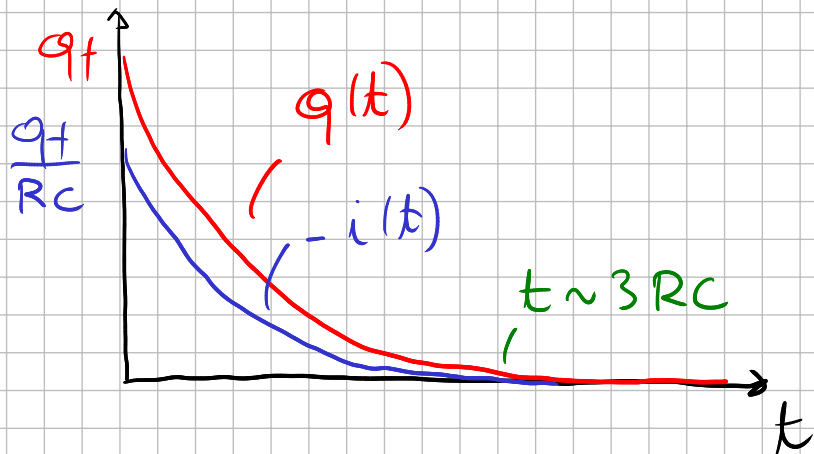
$$\frac{dq}{q} = - \frac{dt}{RC} \Rightarrow q(t) = \underline{q_f} e^{-\frac{t}{RC}}, \quad i(t) = - \frac{q_f}{RC} e^{-\frac{t}{RC}}$$




all'initio $U_e^{(i)} = \frac{1}{2} \frac{q_f^2}{C}$, ma $U_e^{(f)} = 0$

$$P_R = Ri^2 = \frac{q_f^2}{R^2 C^2} e^{-2\frac{t}{RC}} \Rightarrow$$

$$W_R = \int_0^{\infty} \frac{q_f^2}{R^2 C^2} e^{-2\frac{t}{RC}} dt = - \frac{q_f^2 RC}{2RC^2} e^{-\frac{2t}{RC}} \Big|_0^{\infty} =$$

$$= \frac{1}{2} \frac{q_f^2}{C}$$

CENNI SULLE RETI ELETTRICHE

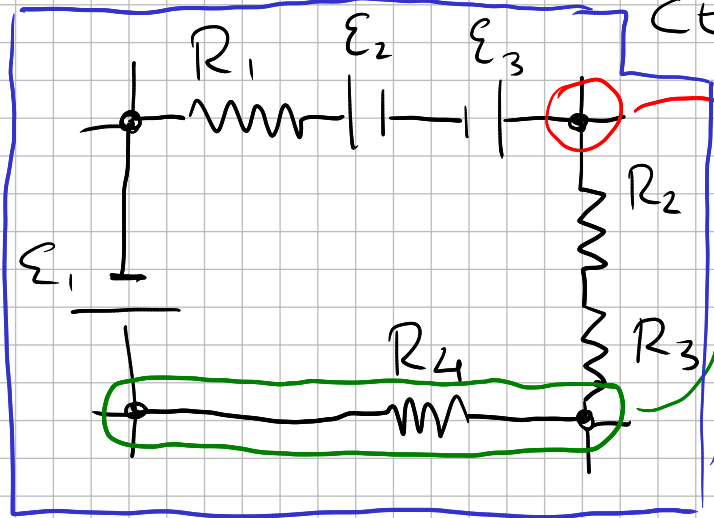


NODO DELLA RETE

RAMO DELLA RETE

MAGLIA DELLA RETE

I LEGGE DI KIRCHHOFF

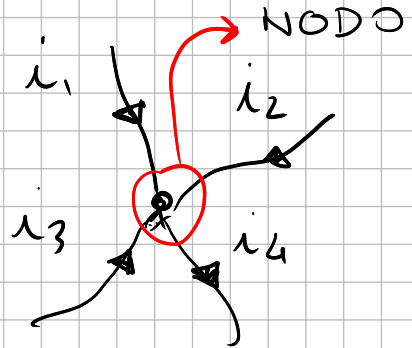


$$\sum_{k=1}^N i_k = 0$$

ATTENZIONE: le correnti devono avere il segno appropriato!

II LEGGE DI KIRCHHOFF


SI APPLICA ALLE MAGLIE

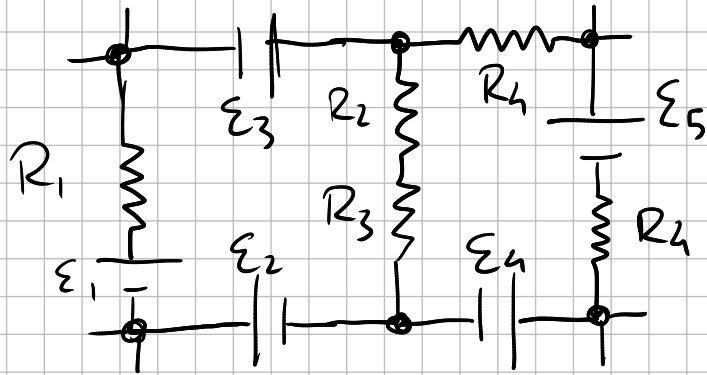

- 1) scegliete una maglia composta da N rami
- 2) scegliete un verso di percorrenza
- 3) vale

$$\sum_{k=1}^N \mathcal{E}_k = \sum_{k=1}^N R_k I_k$$

ESEMPIO

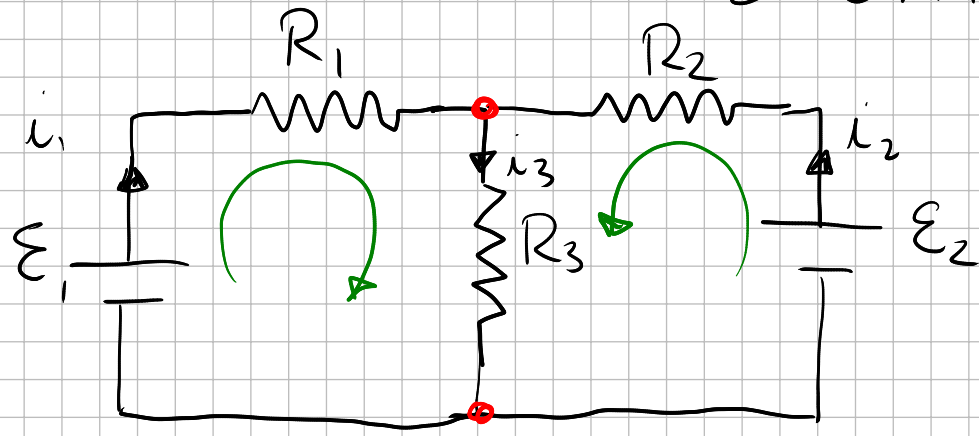

$$\mathcal{E}_1 = 10V, \quad \mathcal{E}_2 = 20V$$

$$R_1 = 10\Omega, \quad R_2 = 20\Omega, \quad R_3 = 40\Omega$$

$$\begin{cases} i_1 + i_2 - i_3 = 0 \\ -i_1 - i_2 + i_3 = 0 \end{cases} \quad \text{I LEGGE}$$

$$\begin{cases} +\mathcal{E}_1 = R_1 i_1 + R_3 i_3 \\ +\mathcal{E}_2 = R_2 i_2 + R_3 i_3 \end{cases} \quad \text{II LEGGE}$$

$$i_1 = -0.143A, \quad i_2 = 0.429A, \quad i_3 = 0.286A$$